
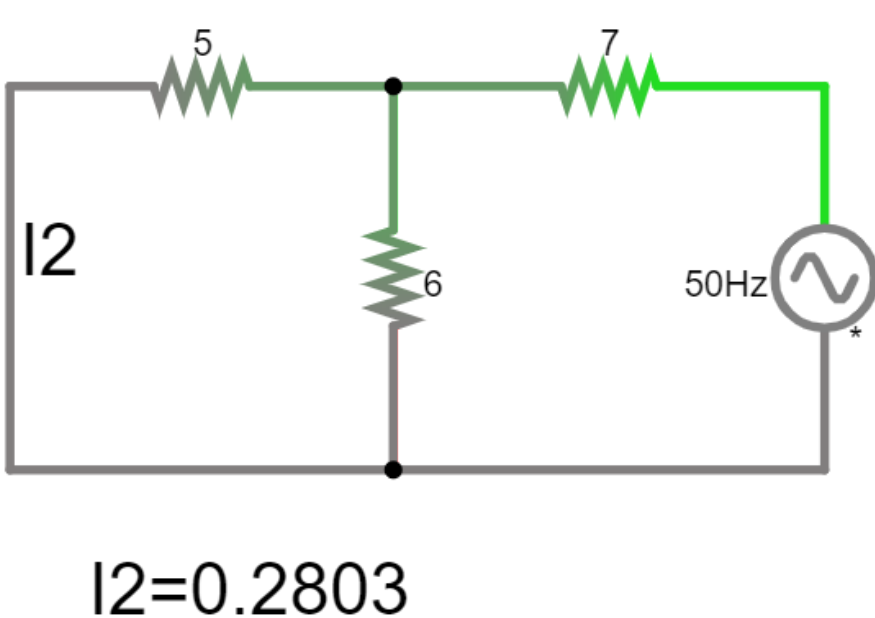


# Experiment No. 03: Verification of Reciprocity Theorem for AC circuit

Question: Verify the Reciprocity Theorem

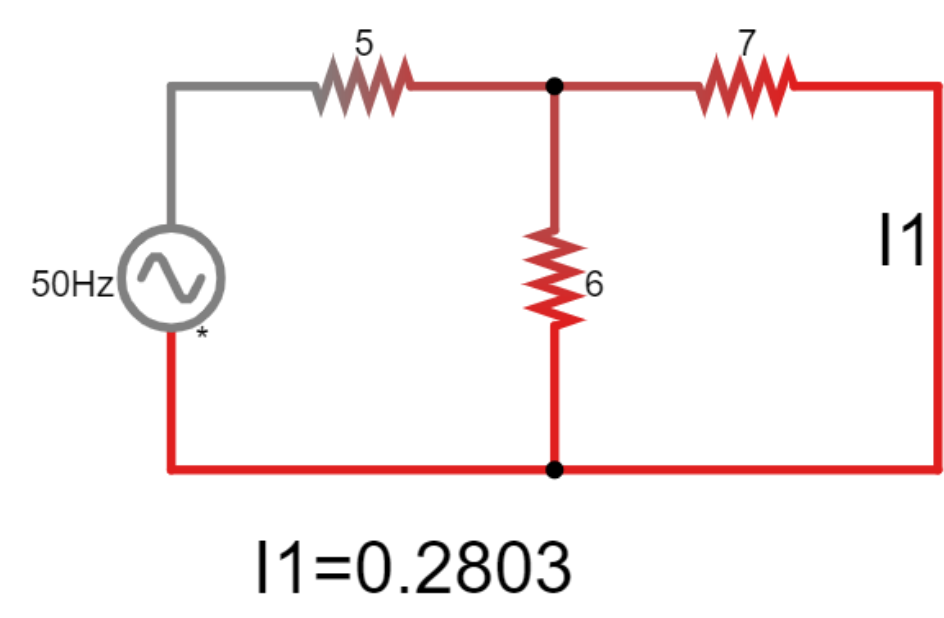

$I_1=I_2=0.2803\text{ A}$

Reciprocity Theorem is Verified

Name - Sagar Thorkar  
Roll no- 72